

**Professional Course Examination, November 2018**

( 1st Semester )

**BACHELOR OF COMPUTER APPLICATIONS**

Course : BCA-104

**( Digital Computer Fundamentals )**

( Revised )

Full Marks : 75

Time : 3 hours

**( PART : A—OBJECTIVE )**

( Marks : 25 )

*The figures in the margin indicate full marks for the questions***SECTION—A**

( Marks : 15 )

Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The 9's complement of  $(636)_{10}$  is

- (a) 336 ( )
- (b) 363 ( )
- (c) 663 ( )
- (d) 373 ( )



2. When an input electrical signal  $A = 10100$  is applied to a NOT gate, its output signal is

- (a) 01011 ( )
- (b) 10001 ( )
- (c) 10101 ( )
- (d) 00101 ( )

3. Conversion of binary number  $101101_2$  to hexadecimal is

- (a)  $37_{16}$  ( )
- (b)  $2E_{16}$  ( )
- (c)  $27_{16}$  ( )
- (d)  $2D_{16}$  ( )

4. Flip-flop outputs are always

- (a) the same ( )
- (b) independent of each other ( )
- (c) complimentary ( )
- (d) same as inputs ( )

5. A half-adder adds \_\_\_\_\_ bits.

- (a) 16 ( )
- (b) 8 ( )
- (c) 4 ( )
- (d) 2 ( )



6. A demultiplexer is also known as

(a) data selector ( )

(b) data distributor ( )

(c) decoder ( )

(d) encoder ( )

7. A shift register can be used for

(a) parallel to serial conversion ( )

(b) serial to parallel conversion ( )

(c) digital delay line ( )

(d) All of the above ( )

8. Binary Coded Decimal (BCD) numbers express each digit as a

(a) byte ( )

(b) bit ( )

(c) nibble ( )

(d) None of the above ( )

9. Multiplication of  $111_2$  by  $101_2$  is

(a)  $110011_2$  ( )

(b)  $100011_2$  ( )

(c)  $111100_2$  ( )

(d)  $000101_2$  ( )



**10.** A combinational logic circuit that selects one of several digit inputs and forwards the selected input into a single line is

- (a) multiplexer ( )
- (b) decoder ( )
- (c) encoder ( )
- (d) demultiplexer ( )

Indicate whether the following statements are *True (T)* or *False (F)* by putting a Tick (✓) mark in the brackets provided : 1×5=5

**1.** A decoder is used to change a BCD number into an equivalent decimal number.

( T / F )

**2.** The hexadecimal number system is widely used in analyzing and programming microprocessor.

( T / F )

**3.** The D flip-flop is a modification of R-S flip-flop.

( T / F )

**4.** A BCD counter is a decade counter.

( T / F )

**5.** An OR gate output is low only if all the inputs are high.

( T / F )



SECTION—B

( Marks : 10 )

Answer the following questions :

2×5=

1. Differentiate between register and counter.
2. Simplify  $(C + D')(C + D)$ .
3. Explain overflow.
4. From the given expression, draw the logic symbol and truth table :

$$\text{Exp} = A + B' \cdot C' + D$$

5. What is encoder?



( PART : B—DESCRIPTIVE )

( Marks : 50 )

The figures in the margin indicate full marks for the questions

1. (a) Convert the following : 6

(i)  $(17)_{10} = (?)_2$

(ii)  $(101011)_2 = (?)_{10}$

(iii)  $(7013)_8 = (?)_{10}$

(b) Explain the  $r$ 's compliment and  $(r - 1)$ 's compliment. What is the 10's compliment of  $(0.3267)_{10}$ ? 4

OR

(c) Write the block diagram of a digital computer and explain its unit. 6

(d) Convert  $(100101100101101011)_2$  to octal and hexadecimal numbers. 4

2. (a) Explain any five digital logic gates with names, graphic symbols and truth table. 5

(b) Simplify the following expression, using four variable  $K$ -map in sum of product form : 5

$$f(A, B, C, D) = \Sigma(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$$

OR

(c) Draw the logic circuit for  $Y = ABC + ABC'$ . Simplify the equation with Boolean algebra and draw the simplified logic circuit. 6

(d) Express the Boolean function  $F = x + yz$  in a sum of minterm form. 4

3. (a) What is multiplexer? Write the logic and draw the block diagram of a 4-to-1 line multiplexer. 6

(b) Explain half-adder by showing its truth table and implementation using logic gates. 4

OR

(c) What is decoder? Design a 3-to-8 line decoder showing its truth table. 6

(d) Explain demultiplexer with suitable diagram. 4



4. (a) Explain the working of J-K flip-flop giving its logic diagram and its characteristics table.

(b) Explain shift register with block diagram.

**OR**

(c) Explain the working of R-S flip-flop giving its logic diagram and its characteristics table.

(d) Differentiate between asynchronous counter and synchronous counter.

5. (a) Explain the following :

(i) Arithmetic micro operation

(ii) Logic micro operation

(iii) Shift micro operation

(b) Differentiate between bus transfer and memory transfer.

**OR**

(c) Explain macro operation and micro operation with diagram.

(d) Differentiate between fixed point binary data and floating point data.