

**I/BCA/104 (R)**

**2014**

( 1st Semester )

**BACHELOR OF COMPUTER APPLICATION**

Paper No. : BCA-104

( Revised )

**( Digital Computer Fundamentals )**

( PART : A—OBJECTIVE )

( Marks : 25 )

*The figures in the margin indicate full marks for the questions*

**SECTION—I**

( Marks : 15 )

**I. Tick (✓) the correct answer in the brackets provided :**

1×10=10

1.  $(1)_{10} + (1)_{10}$  equals to

(a) 2 ( )

(b) 0 ( )

(c) 1 ( )

(d) 10 ( )

( 2 )


2. The 1's complement of  $(1000)_2$  is

(a) 0111 ( )

(b) 0101 ( )

(c) 1000 ( )

(d) 0001 ( )

3.  is a symbol for

(a) NAND gate ( )

(b) NOR gate ( )

(c) AND gate ( )

(d) OR gate ( )

4. For a Boolean expression,  $F = xyz$ , the value of  $F$  will be 1, if

(a)  $x = 0, y = 0, z = 0$  ( )

(b)  $x = 0, y = 0, z = 1$  ( )

(c)  $x = 0, y = 1, z = 1$  ( )

(d)  $x = 1, y = 1, z = 1$  ( )

( 3 )

5. A combinational circuit that performs the addition of two bits is called

(a) half adder ( )

(b) full adder ( )

(c) half subtractor ( )

(d) full subtractor ( )

6. A digital function that produces the arithmetic sum of two binary numbers in parallel is

(a) full adder ( )

(b) binary parallel adder ( )

(c) decimal adder ( )

(d) BCD adder ( )

7. A register is a group of

(a) OR gates ( )

(b) OR and AND gates ( )

(c) flip-flops ( )

(d) None of the above ( )

( 4 )

8. A register that goes through a predetermined sequence of states is called

(a) counter ( )

(b) flip-flop ( )

(c) RAM ( )

(d) T-register ( )

9. MAR stands for

(a) Main Architecture Register ( )

(b) Multi Addition Register ( )

(c) Memory Argument Register ( )

(d) Memory Address Register ( )

10. The symbol R2 denotes

(a) a register ( )

(b) bit of a register ( )

(c) transfer of information ( )

(d) control function ( )

( 5 )

II. Tick (✓) whether the following statements are  
True (T) or False (F) :  $1 \times 5 = 5$

1. Using 2's complement subtraction,  
 $(1010100)_2 - (1000100)_2$  is  $0010000$ .

( T / F )

2. A primed variable is not a literal.

( T / F )

3. Multiplexer means one-to-many.

( T / F )

4. A flip-flop circuit loses its state as soon as power  
is not delivered to the circuit.

( T / F )

5. A memory register of word is symbolized by the  
letter M.

( T / F )

( 6 )

SECTION—II

( Marks : 10 )

III. Answer the following questions :

2×5=10

1. What is a register?

( 7 )

2. Write the gate symbol and truth table for Exclusive-OR (XOR) operation.

3. What is half subtractor?

( 8 )

4. What is a flip-flop?



( 9 )

5. What is an overflow?

\*\*\*

**I/BCA/104 (R)**

**2014**

**( 1st Semester )**

**BACHELOR OF COMPUTER APPLICATION**

**Paper No. : BCA-104**

**( Revised )**

**( Digital Computer Fundamentals )**

*Full Marks : 75*

*Time : 3 hours*

**( PART : B—DESCRIPTIVE )**

*( Marks : 50 )*

*The figures in the margin indicate full marks  
for the questions*

Answer the following questions : 10×5=50

1. (a) What are the error detection codes? Give example. 4

(b) Convert  $(1000111101010000)_2$  to hexadecimal, octal and decimal numbers. 6

*Or*

(c) Define binary logic. Also explain the three basic operations of binary logic. 5

(d) Convert  $(41)_{10}$  to binary, hexadecimal and octal numbers. 5

G15—280/192a

*( Turn Over )*

2. (a) Using Karnaugh's four-variable mapping, simplify the Boolean function

$$F = A'B'C' + B'CD' + A'BCD' + AB'C' \quad 6$$

- (b) Write the gate implementation for the function  $F = xy + x'y'$ . 4

Or

- (c) Express the Boolean function  $F = xy + x'z$  in a product of maxterm form. 5

- (d) Using Karnaugh's three-variable mapping, simplify the Boolean function

$$F = x'yz + x'yz' + xy'z' + xy'z \quad 5$$

3. (a) What is a decoder? Write and explain a 3-to-8 line decoder. 5

- (b) Explain half adder by showing its truth table and implementation using logic gates. 5

Or

- (c) What is a multiplexer? Write the logic diagram and block diagram of a 4-to-1 line multiplexer. 5

- (d) Explain full adder by showing its truth table and implementation using logic gates. 5

4. (a) Explain the working of *D* flip-flop giving its logic diagram with NAND gates and its characteristic table. 5
- (b) Describe how a shift register works by giving a detailed block diagram. 5

Or

- (c) Explain the working *J-K* flip-flop giving its logic diagram and its characteristic table. 5
- (d) What is a ripple counter? Explain how it works by giving a neat diagram. 5

5. (a) Explain different types of micro-operation encountered in digital systems. 5
- (b) Differentiate between logic micro-operation and shift microoperation by giving a suitable example. 5

Or

- (c) Explain the procedure for addition with sign 2's complement and sign 1's complement representation by giving a suitable example. 6
- (d) Explain arithmetic shift operation with a suitable example. 4

\*\*\*