

I/BCA/104

2016

(1st Semester)

BACHELOR OF COMPUTER APPLICATION

Paper No. : BCA-104

(Digital Computer Fundamentals)

Full Marks : 75

Time : 3 hours

(PART : B—DESCRIPTIVE)

(Marks : 50)

*The figures in the margin indicate full marks
for the questions*

1. (a) Explain any five digital logic gates with names, graphic symbols and truth tables. 5
- (b) Convert $(10110001101011)_2$ to decimal, octal and hexadecimal. 5
- Or*
- (c) Define binary logic. Also explain the three basic operators of binary logic. 5

G7/180a

(Turn Over)

- (d) Convert $(45)_{10}$ to binary, octal and hexadecimal. 5
2. (a) Simplify the Boolean function $F = x \cdot y + x' \cdot z + y \cdot z$ to a minimum number of literals. 4
- (b) Express the Boolean function $F = xy + x'z$ in a product of maxterm form. 6

Or

- (c) Using Karnaugh's three-variable mapping, simplify the Boolean function $F = x'yz + x'yz' + xy'z' + xy'z$ 5
- (d) Express the Boolean function $F = x + y'z$ in a sum of minterm form. 5
3. (a) What is multiplexer? Write the logic and block diagram of a 4-to-1 line multiplexer. 5
- (b) Explain full adder by showing its truth table and implementation using logic gates. 5

Or

- (c) What is decoder? Design a 3-to-8 lines decoder showing its truth table. 5
- (d) Explain full subtractor by showing its truth table and implementing using logic gates. 5

4. (a) Explain the working of JK flip-flop giving its logic diagram and its characteristics table. 6
- (b) Explain shift register with block diagram. 4
- Or*
- (c) Explain the working of RS flip-flop with logical diagram and its characteristic table. 5
- (d) What is ripple counter? Explain how it works showing suitable diagram. 5
5. (a) Explain macrooperations and microoperations with an example. 6
- (b) Explain arithmetic shift operation with a suitable example. 4
- Or*
- (c) Differentiate between logic microoperation and shift microoperation by giving suitable example. 5
- (d) Explain briefly the basic arithmetic microoperations in detail. 5

2016

(1st Semester)

BACHELOR OF COMPUTER APPLICATION

Paper No. : BCA-104

(**Digital Computer Fundamentals**)

(PART : A—OBJECTIVE)

(Marks : 25)

The figures in the margin indicate full marks for the questions

SECTION—I

(Marks : 15)

I. Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The binary form of $(27)_{10}$ is

(a) 10110 ()

(b) 11011 ()

(c) 11100 ()


(d) 10101 ()

2. A combinational circuit that performs the addition of two bits is called

- (a) half adder ()
- (b) full adder ()
- (c) half subtractor ()
- (d) full subtractor ()

3. A flip-flop circuit that can be constructed from two NAND gates and two NOR gates is called

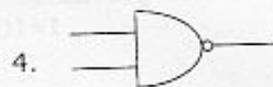- (a) JK flip-flop ()
- (b) D flip-flop ()
- (c) RS flip-flop ()
- (d) J flip-flop ()



is a symbol for

- (a) .AND ()
- (b) OR ()
- (c) .NOR ()
- (d) NAND ()

5. A combinational circuit that selects binary information from one of many input lines and directs it to a single output line is called

(a) multiplexer ()

(b) demultiplexer ()

(c) decoder ()

(d) encoder ()

6. The 2's complement of $(101100)_2$ is

(a) 010011 ()

(b) 010100 ()

(c) 110011 ()

(d) 001101 ()

7. MBR stands for

(a) main buffer register ()

(b) multi buffer register ()

(c) memory buffer register ()

(d) None of the above ()

8. The D flip-flop is a modification of the

- (a) JK flip-flop ()
- (b) RS flip-flop ()
- (c) clocked JK flip-flop ()
- (d) clocked RS flip-flop ()

9. Ripple counters are sometimes called

- (a) asynchronous counters ()
- (b) synchronous counters ()
- (c) program counters ()
- (d) registers ()

10. $(1)_{10} + (1)_{10}$ equals to

- (a) 0 ()
- (b) 1 ()
- (c) 2 ()
- (d) 10 ()

(5)

II. Tick (✓) whether the following statements are
True (T) or False (F) : 1×5=5

1. A register is a group of binary storage cells suitable for holding binary informations.

(T / F)

2. An encoder is a combinational circuit that connects binary information from n input lines to a maximum of 2^n unique output lines.

(T / F)

3. Demultiplexer means one-to-many.

(T / F)

4. The maximum number of bits required to code 2^n distinct quantities is n .

(T / F)

5. The T flip-flop is a single input version of the RS flip-flop.

(T / F)

(6)

SECTION—II

(Marks : 10)

III. Answer the following questions : 2×5=10

1. What do you mean by overflow?

(7)

2. Explain half adder in detail.

3. From the given expression, draw the gate symbol and truth table :

$$\text{Exp.} = A + B + \bar{C}$$

4.- What is flip-flop?

(9)

5. What is register?
